
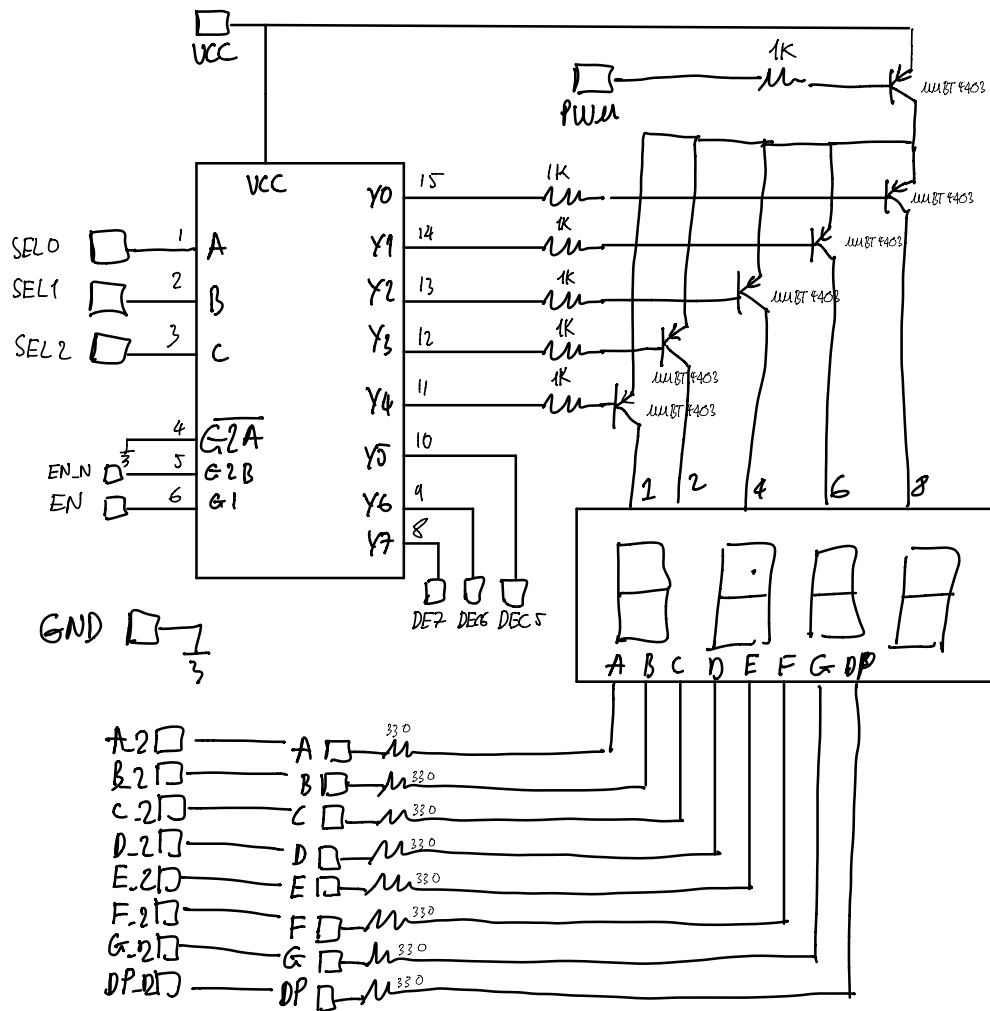



# 4 LED BOARD.

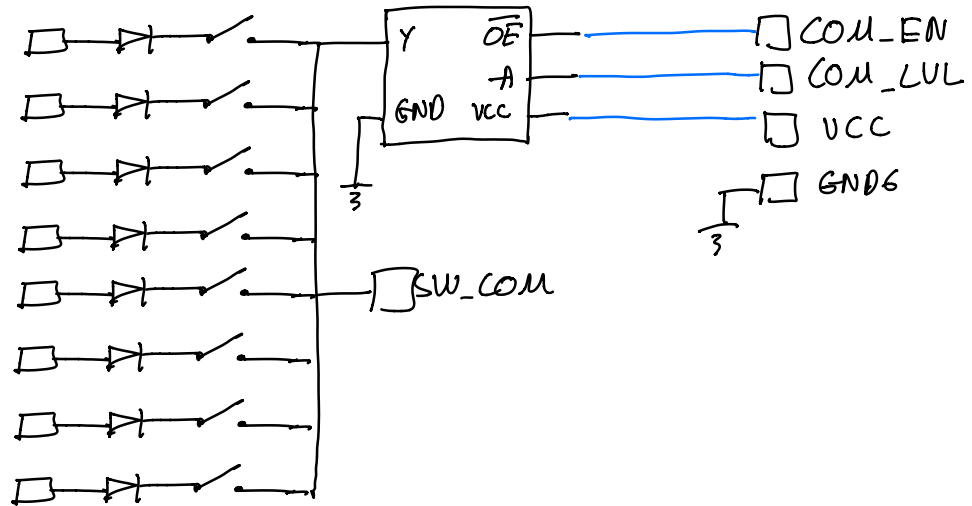


## Push Button Board



## Schematic

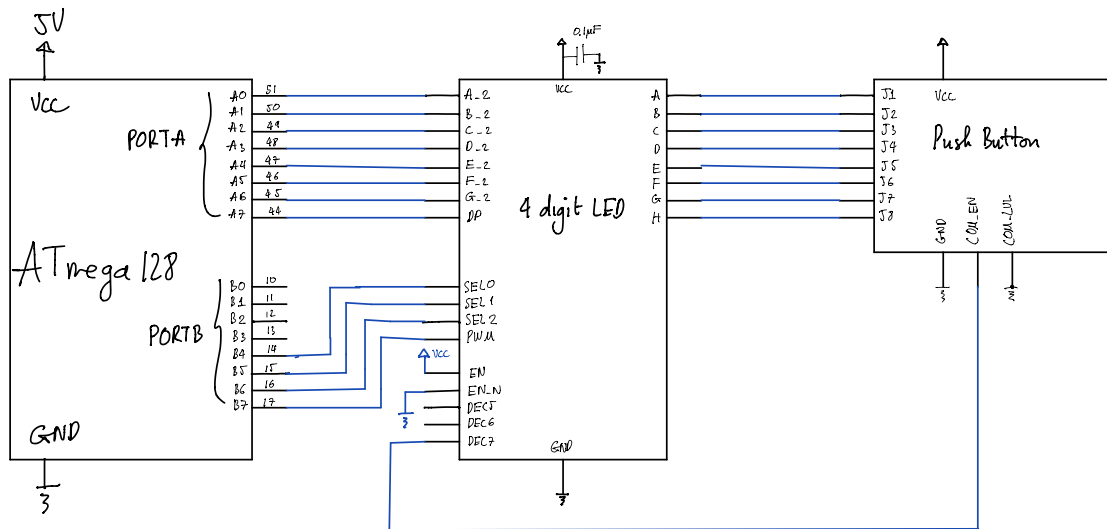

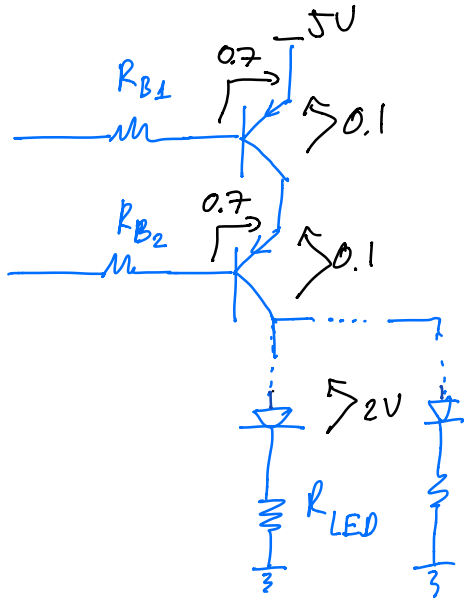

According to the datasheet of the LED,  
continuous current per each segment =  $20\text{mA}$

voltage drop across the LED is  $2\text{V}$

$$I = 20\text{mA}$$

$$V_{\text{led}} = 2\text{V}$$

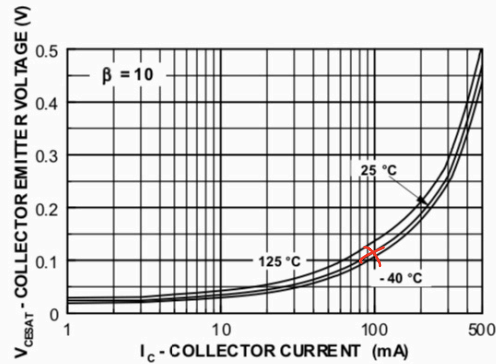


Figure 4. Collector-Emitter Saturation Voltage vs. Collector Current

We can drive up to 8 segments with 1 BJT

$$I_{\text{max}} = 20\text{mA} \times 8 = 160\text{mA}$$

Let adjust our calculation to allow only 100mA

$$\Rightarrow V_{\text{CE}} = 0.1\text{V}$$

Calculating voltage drop across  $R_{\text{LED}}$

$$V_{R_{\text{led}}} = 5 - 0.1 \times 2 - 2 = 2.8\text{V}$$

$$\Rightarrow R_{\text{led}} = \frac{2.8}{100\text{mA} / 8} = \underline{\underline{224\Omega}}$$

closest in the box is  $330\Omega$

$$\Rightarrow I_{\text{LED with } R=330\Omega} = 8.4\text{mA}$$

$$R_{\text{LED}} = 330\Omega$$

- 1] The sum of all IOL, for all ports, should not exceed 400mA.
- 2] The sum of all IOL, for ports A0 - A7, G2, C3 - C7 should not exceed 100mA.
- 3] The sum of all IOL, for ports C0 - C2, G0 - G1, D0 - D7, XTAL2 should not exceed 100mA.
- 4] The sum of all IOL, for ports B0 - B7, G3 - G4, E0 - E7 should not exceed 100mA.

if  $R_{LED}$  is  $330\Omega \Rightarrow I_{LED} = 8.4 \text{ mA}$

$I_{8 \text{ LEDs}} = 67.2 \text{ mA} < 100 \text{ mA}$

Port A is OK to drive all 8 LEDs (include the dot)

★ For the  $R_{B2}$ , we have  $\beta = 10$

$$I_C = 58.8 \text{ mA} \Rightarrow I_B \approx \frac{I_C}{\beta} = 5.88 \text{ mA}$$

$$|V_{BE}| = 0.7 \text{ V} \leftarrow \text{voltage drop across emitter-base}$$

$$\Rightarrow V_{R_{B2}} = 5 - 0.1 - 0.7 = 4.2 \text{ V}$$

$$\Rightarrow R_{B2} = \frac{4.2}{5.88 \text{ mA}} = 0.714 \text{ k}\Omega$$

closest is  $1 \text{ k}\Omega$

We will only drive one digit at a time

$$\Rightarrow R_{B2} = R_{B1} = 1 \text{ k}\Omega$$

---

Recheck for saturation  $I_B = \frac{5 - 0.7}{1 \text{ k}} = 4.3 \text{ mA}$

$$h_{FE_{min}} = 100 > \frac{I_C}{I_B} = 3 \quad \Rightarrow \quad I_C = I_B + I_{LED} = 12.7 \text{ mA}$$

@  $I_C = 150 \text{ mA}$

$$h_{FE_{min}} = 100 > \frac{I_C}{I_B} = 16.7 \quad \Rightarrow \quad I_C = I_B + I_{LED} \times 8 = 71.8 \text{ mA}$$

@  $I_C = 150 \text{ mA}$

BJT always in saturation

checking for LED visibility

We are pushing 8.4 mA  
through each LED

$\Rightarrow$  relative lumen intensity = 0.8

$\Rightarrow$  lumen intensity =  $0.8 \times 650$   
 $= 520 \mu\text{cd}$

Also, the LED is delayed for 1 ms each pulse for  
human eyes.

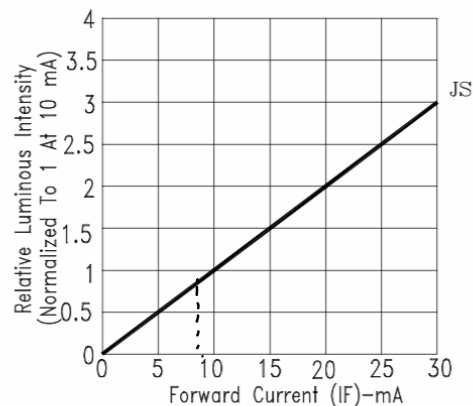


Fig4. RELATIVE LUMINOUS INTENSITY  
VS. FORWARD CURRENT